

Verilog Review

Lecture 03

Josh Brake

Harvey Mudd College

Outline

- Verilog tips
- Design guidelines and basic idioms
- Bad Verilog Examples/Bug finding

Learning Objectives

By the end of this lecture you should be able to...

- Recall basic Verilog idioms for common digital structures
- Analyze Verilog code to find errors

Verilog Tips

- Think about _____ you want, write code that implies it. Use the _____ and never think about this as coding.
- Watch for _____ in tool. Take them seriously – often a sign of a big problem.
- _____ : draw box with inputs, outputs. Divide into simpler boxes until you can understand it.

Design Guidelines and Idioms for Common Structures

- Simple combinational logic: use _____
- For a mux: _____
- Truth tables: `always_comb` and _____ (default case of x)
- Finite state machines. Three portions: _____, _____, _____.
- Use _____, _____, not plain always blocks.
- Use _____ datatype everywhere except on tristates, and don't use tristates

System Verilog Operators

Listed in order of descending precedence. Operators sharing a precedence number are evaluated left to right.

Prec.	Operator	Name	Functional group
1	[]	bit-select or part-select	
2	()	parentheses	
3	!	logical negation	logical
3	~	negation	bit-wise
3	&	reduction AND	reduction
3		reduction OR	reduction
3	~&	reduction NAND	reduction
3	~	reduction NOR	reduction
3	^	reduction XOR	reduction
3	~^ or ^~	reduction XNOR	reduction
4	+	unary (sign) plus	arithmetic
4	-	unary (sign) minus	arithmetic
5	{ }	concatenation	concatenation
6	{ { } }	replication	replication
7	*	multiply	arithmetic
7	/	divide	arithmetic
7	%	modulus	arithmetic
8	+	binary plus	arithmetic
8	-	binary minus	arithmetic

Prec.	Operator	Name	Functional group
9	<<	shift left	shift
9	>>	shift right	shift
10	>	greater than	relational
10	>=	greater than or equal to	relational
10	<	less than	relational
10	<=	less than or equal to	relational
11	==	logical equality	equality
11	!=	logical inequality	equality
12	===	case equality	equality
12	!==	case inequality	equality
13	&	bit-wise AND	bit-wise
14	^	bit-wise XOR	bit-wise
14	~^ or ^~	bit-wise XNOR	bit-wise
15		bit-wise OR	bit-wise
16	&&	logical AND	logical
17		logical OR	logical
18	?:	conditional	conditional

Harris and Harris, *Digital Design and Computer Architecture*, ARM Ed., p. 185

Bad Verilog: Learning by Counter Example

Bad Verilog Example #1

```
1 module mux(input logic [3:0] d0, d1,  
2             input logic      s,  
3             output logic [3:0] y);  
4     always_comb @(posedge s)  
5         if (s) y <= d1;  
6         else  y <= d0;  
7 endmodule
```


Bad Verilog Example #2

```
1 module mux2(input logic [3:0] d0, d1,  
2             input logic      s,  
3             output           [3:0] y);  
4  
5     tristate t0(d0, s, y);  
6     tristate t1(d1, s, y);  
7 endmodule
```

Bad Verilog Example #3

```
1 module mux3(input logic [3:0] d0, d1, d2,  
2             input logic [1:0] s,  
3             output logic [3:0] y);  
4  
5     always @(*)  
6         if (s == 2'b00) y <= d0;  
7         else if (s == 2'b01) y <= d1;  
8         else if (s == 2'b10) y <= d2;  
9     endmodule
```

Bad Verilog Example #4

```
1 module mux8(input logic [3:0] d0, d1, d2, d3, d4, d5, d6, d7,  
2             input logic [2:0] s,  
3             output logic [3:0] y);  
4  
5     always_comb  
6     case (s)  
7         1'd0: y <= d0;  
8         1'd1: y <= d1;  
9         1'd2: y <= d2;  
10        1'd3: y <= d3;  
11        1'd4: y <= d4;  
12        1'd5: y <= d5;  
13        1'd6: y <= d6;  
14        1'd7: y <= d7;  
15        default: y <= 4'bxxxx;  
16    endcase  
17 endmodule
```

Bad Verilog Example #5

```
1 module and3(input logic a, b, c,  
2             output logic y);  
3  
4     logic tmp;  
5  
6     always @(a, b, c)  
7     begin  
8         tmp <= a & b;  
9         y <= tmp & c;  
10    end  
11 endmodule
```

Bad Verilog Example #6

```
1 module counter(input logic clk,  
2                 output logic [31:0] q);  
3  
4     always_ff @(posedge clk)  
5         q <= q+1;  
6 endmodule
```

Bad Verilog Example #7

```
1 module counter2(input logic clk,  
2                 output logic [31:0] q);  
3     initial q <= 32'b0;  
4  
5     always_ff @(posedge clk) q <= q+1;  
6 endmodule
```

Bad Verilog Example #8

```
1 module gates(input logic [3:0] a, b,  
2               output logic [3:0] y1, y2, y3, y4, y5);  
3  
4     always @(a)  
5         begin  
6             y1 <= a & b; // AND  
7             y2 <= a | b; // OR  
8             y3 <= a ^ b; // XOR  
9             y4 <= ~(a & b); // NAND  
10            y5 <= ~(a | b); // NOR  
11        end  
12    endmodule
```

Bad Verilog Example #9

```
1 module priority_always(input logic [3:0] a,  
2                        output logic [3:0] y);  
3  
4     // a 4-input priority encoder  
5     always @(*)  
6         if      (a[3]) y <= 4'b1000;  
7         else if (a[2]) y <= 4'b0100;  
8         else if (a[1]) y <= 4'b0010;  
9         else if (a[0]) y <= 4'b0001;  
10    endmodule
```


Bad Verilog Example #10

```
1 module seven_seg_display_decoder(input logic [3:0] data,  
2                                 output logic [6:0] segments);  
3     always @(*)  
4         case (data)  
5             0: segments <= 7'b000_0000; // ZERO  
6             1: segments <= 7'b111_1110; // ONE  
7             2: segments <= 7'b011_0000; // TWO  
8             3: segments <= 7'b110_1101; // THREE  
9             4: segments <= 7'b011_0011; // FOUR  
10            5: segments <= 7'b101_1011; // FIVE  
11            6: segments <= 7'b101_1111; // SIX  
12            7: segments <= 7'b111_0000; // SEVEN  
13            8: segments <= 7'b111_1111; // EIGHT  
14            9: segments <= 7'b111_1011; // NINE  
15        endcase  
16    endmodule
```

Bad Verilog Example #11

```
1 module latch(input logic clk,  
2               input logic [3:0] d,  
3               output logic [3:0] q);  
4  
5     always_latch @(clk)  
6         if (clk) q <= d;  
7 endmodule
```

Bad Verilog Example #12

```
1 module floprsen(input logic clk,  
2                 input logic reset,  
3                 input logic set,  
4                 input logic [3:0] d,  
5                 output logic [3:0] q);  
6  
7     always_ff @(posedge clk, posedge reset)  
8         if (reset) q <= 0;  
9         else      q <= d;  
10  
11     always @(set)  
12         if (set) q <= 1;  
13 endmodule
```

Bad Verilog Example #13

```
1 module twobitflop(input logic clk,  
2                   input logic [1:0] d,  
3                   output logic [1:0] q);  
4  
5     always_ff @(posedge clk)  
6         q[1] = d[1];  
7         q[0] = d[0];  
8 endmodule
```

Bad Verilog Example #14

```
1 module FSMbad(input logic clk,  
2               input logic a,  
3               output logic out1, out2);  
4  
5     logic state;  
6  
7     always_ff @(posedge clk)  
8         if (state == 0) begin  
9             if (a) state <= 1;  
10        end else begin  
11            if (~a) state <= 0;  
12        end  
13  
14     always @(*)  
15         if (state == 0) out1 <= 1;  
16         else out2 <= 1;  
17 endmodule
```

Bad Verilog Example #15

```
1 module divideby3counter(input logic    clk, reset,  
2                          output logic [1:0] q);  
3  
4     always_ff @(posedge clk or posedge reset)  
5         if (reset) q = 0;  
6         else begin  
7             q = q+1;  
8             if (q == 2) q = 0;  
9         end  
10    endmodule
```

Bad Verilog Example #16

```
1 module divideby3FSM(input logic clk,  
2                     input logic reset,  
3                     output logic out);  
4  
5     logic [1:0] state, nextstate;  
6  
7     parameter S0 = 2'b00;  
8     parameter S1 = 2'b01;  
9     parameter S2 = 2'b10;  
10  
11     // State Register  
12     always_ff @(posedge clk, posedge reset)  
13         if (reset) state <= S0;  
14         else state <= nextstate;  
15 // Next State Logic  
16 always @(*)  
17     case (state)  
18         S0: nextstate <= S1;  
19         S1: nextstate <= S2;  
20         S2: nextstate <= S0;  
21     endcase  
22  
23     // Output Logic  
24     assign out = (state == S2);  
25 endmodule
```

Bad Verilog Example #17

```
1 module divideby3FSM2(input logic clk,  
2                       output logic out);  
3  
4     logic [1:0] state, nextstate;  
5  
6     parameter S0 = 2'b00;  
7     parameter S1 = 2'b01;  
8     parameter S2 = 2'b10;  
9  
10    initial state = 2'b00;  
11  
12    // State Register  
13    always_ff @(posedge clk)  
14        if (state == 2'b00) state <= 2'b01;  
15        else if (state == 2'b01) state <= 2'b10;  
16        else if (state == 2'b10) state <= 2'b00;  
17  
18    // Output Logic  
19    assign out = (state == S2);  
20 endmodule
```


Bad Verilog Example #18

```
1 module adventuregameFSM(input      clk, reset, N, S, E, W,
2                          output logic [3:0] room,
3                          output logic  win, die);
4
5   always_ff @(posedge clk or posedge reset)
6   if (reset) begin
7       room <= 4'b0001;
8       die <= 0;
9       win <= 0;
10      end
11
12      else case (room)
13          4'b0001: if (E) room <= 4'b0010;
14                  else die <= 1;
15          4'b0010: if (S) room <= 4'b0100;
16                  if (W) room <= 4'b0001;
17                  else die <= 1;
18          4'b0100: if (E) room <= 4'b1000;
19                  if (N) room <= 4'b0010;
20                  else die <= 1;
21      endcase
22  always_comb
23  if (room == 4'b1000) win <= 1;
24 endmodule
```

Where Did Each Bug Bite?

Compiler, simulation, or the board? Sort them.

Wrap Up

- Think about hardware you want. Then write the HDL to imply the proper logic.
- Check the Netlist Analyzer to ensure that the tool is inferring the logic you are intending.
- Make sure to not infer latches.

Announcements and Reminders